

Verilog Lab Week #1

1. “Hello World” in Verilog

```
//-----  
  
// This is my first Verilog Program  
  
// Design Name : hello_world  
  
// File Name : hello_world.v  
  
// Function : This program will print 'hello world'  
  
//-----  
  
module helloWorld;  
  
    initial begin  
  
        $display ("Hello World!!!");  
  
        #10 $finish;  
  
    end  
  
endmodule // End of Module helloWorld
```

Results

```
[2024-09-24 06:35:47 UTC] iverilog '-wall' '-g2012' design.sv testbench.sv && unbuffer vvp a.out  
Hello World!!!  
design.sv:10: $finish called at 10 (1s)  
Finding VCD file...  
No *.vcd file found. EPWave will not open. Did you use '$dumpfile("dump.vcd"); $dumpvars;'?  
Done
```

2. The digital circuit schematics based on the module gate

Main module “gate”

```
module gates(  
    output wire out0, // Declare outputs  
    output wire out1,
```

```

output wire out2,
input wire in1, // Declare inputs
input wire in2,
input wire in3,
input wire in4
);

// Logic operations
not U1(out0, in1);
and U2(out1, in1, in2, in3, in4);
xor U3(out2, in1, in2, in3);

endmodule

Testbench for gate
// Testbench for the "gates" module
module testbench();

// Inputs to the gates module (reg type for testbench)
reg in1, in2, in3, in4;

// Outputs from the gates module (wire type)
wire out0, out1, out2;

// Instantiate the "gates" module
gates uut (
    .out0(out0),
    .out1(out1),
    .out2(out2),
    .in1(in1),
    .in2(in2),
    .in3(in3),
    .in4(in4)
);

// Test logic
initial begin
    // Display the header
    $display("in1 in2 in3 in4 | out0 out1 out2");
    $display("-----");

```

```

// Apply different input combinations and display results
in1 = 0; in2 = 0; in3 = 0; in4 = 0; #10;
$display("%b %b %b %b | %b %b %b", in1, in2, in3, in4, out0, out1, out2);

in1 = 0; in2 = 1; in3 = 1; in4 = 0; #10;
$display("%b %b %b %b | %b %b %b", in1, in2, in3, in4, out0, out1, out2);

in1 = 1; in2 = 1; in3 = 0; in4 = 1; #10;
$display("%b %b %b %b | %b %b %b", in1, in2, in3, in4, out0, out1, out2);

in1 = 1; in2 = 1; in3 = 1; in4 = 1; #10;
$display("%b %b %b %b | %b %b %b", in1, in2, in3, in4, out0, out1, out2);

$finish;
end
endmodule

```


Results

```

[2024-09-24 17:33:14 UTC] iverilog '-wall' '-g2012' design.sv testbench.sv && unbuffer vvp a.out
in1 in2 in3 in4 | out0 out1 out2
-----
0  0  0  0 | 1  0  0
0  1  1  0 | 1  0  0
1  1  0  1 | 0  0  0
1  1  1  1 | 0  1  1
testbench.sv:40: $finish called at 40 (1s)
Done

```

Digital circuit schematics

 

3. Main Module for oneBitFA1 (Continuous Assignment)

```
module oneBitFA1(  
    input wire a, // Input bit a  
    input wire b, // Input bit b  
    input wire ci, // Input carry-in  
    output wire co, // Output carry-out  
    output wire sum // Output sum  
);  
    // Continuous assignment to calculate sum and carry-out  
    assign {co, sum} = a + b + ci;  
  
endmodule
```

Testbench for oneBitFA1

```
module tb_oneBitFA1;  
    // Inputs  
    reg a, b, ci;  
    // Outputs  
    wire co, sum;  
  
    // Instantiate the full adder module  
    oneBitFA1 uut (  
        .a(a),  
        .b(b),  
        .ci(ci),  
        .co(co),  
        .sum(sum)  
    );  
  
    // Initial block to apply inputs  
    initial begin  
        // Apply different combinations of inputs  
        a = 0; b = 0; ci = 0;  
        #10 a = 0; b = 0; ci = 1;  
        #10 a = 0; b = 1; ci = 0;  
        #10 a = 0; b = 1; ci = 1;
```

```

        #10 a = 1; b = 0; ci = 0;
        #10 a = 1; b = 0; ci = 1;
        #10 a = 1; b = 1; ci = 0;
        #10 a = 1; b = 1; ci = 1;
        #10 $finish; // End the simulation
    end

    // Monitor to display the results
    initial begin
        $monitor("At time %0d: a = %b, b = %b, ci = %b | sum = %b, co = %b", $time, a, b,
ci, sum, co);
    end
endmodule

```

Results

```

[2024-09-24 07:39:03 UTC] iverilog '-wall' '-g2012' design.sv testbench.sv && unbuffer vvp a.out
At time 0: a = 0, b = 0, ci = 0 | sum = 0, co = 0
At time 10: a = 0, b = 0, ci = 1 | sum = 1, co = 0
At time 20: a = 0, b = 1, ci = 0 | sum = 1, co = 0
At time 30: a = 0, b = 1, ci = 1 | sum = 0, co = 1
At time 40: a = 1, b = 0, ci = 0 | sum = 1, co = 0
At time 50: a = 1, b = 0, ci = 1 | sum = 0, co = 1
At time 60: a = 1, b = 1, ci = 0 | sum = 0, co = 1
At time 70: a = 1, b = 1, ci = 1 | sum = 1, co = 1
testbench.sv:27: $finish called at 80 (1s)

```

Main Module for oneBitFA2 (1-bit Full Adder using Always Block)

```

module oneBitFA2 (
    input wire a_i,
    input wire b_i,
    input wire ci_i,
    output reg sum_o,
    output reg co_o
);

    // Always block for sum and carry-out
    always @(*) begin
        {co_o, sum_o} = a_i + b_i + ci_i;
    end
endmodule

```

Testbench for oneBitFA2

```

module tb_oneBitFA2;

    // Declare testbench inputs and outputs
    reg a_i, b_i, ci_i;
    wire sum_o, co_o;

    // Instantiate the oneBitFA2 module
    oneBitFA2 uut (
        .a_i(a_i),
        .b_i(b_i),
        .ci_i(ci_i),
        .sum_o(sum_o),
        .co_o(co_o)
    );

    // Testbench procedure
    initial begin
        $display("Testing 1-bit full adder using always block (oneBitFA2)...");
        $monitor("a_i=%b, b_i=%b, ci_i=%b -> sum_o=%b, co_o=%b", a_i, b_i, ci_i,
sum_o, co_o);

        // Test case 1
        a_i = 0; b_i = 0; ci_i = 0;
        #10;

        // Test case 2
        a_i = 0; b_i = 0; ci_i = 1;
        #10;

        // Test case 3
        a_i = 0; b_i = 1; ci_i = 0;
        #10;

        // Test case 4
        a_i = 0; b_i = 1; ci_i = 1;
        #10;

        // Test case 5
        a_i = 1; b_i = 0; ci_i = 0;
        #10;
    end

```

```

// Test case 6
a_i = 1; b_i = 0; ci_i = 1;
#10;

// Test case 7
a_i = 1; b_i = 1; ci_i = 0;
#10;

// Test case 8
a_i = 1; b_i = 1; ci_i = 1;
#10;

// End simulation
$finish;
end
endmodule

```

Results

```

[2024-09-24 07:44:53 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv && unbuffer vvp a.out
At time 0: a = 0, b = 0, ci = 0 | sum = 0, co = 0
At time 10: a = 0, b = 0, ci = 1 | sum = 1, co = 0
At time 20: a = 0, b = 1, ci = 0 | sum = 1, co = 0
At time 30: a = 0, b = 1, ci = 1 | sum = 0, co = 1
At time 40: a = 1, b = 0, ci = 0 | sum = 1, co = 0
At time 50: a = 1, b = 0, ci = 1 | sum = 0, co = 1
At time 60: a = 1, b = 1, ci = 0 | sum = 0, co = 1
At time 70: a = 1, b = 1, ci = 1 | sum = 1, co = 1
testbench.sv:27: $finish called at 80 (1s)
Done

```